
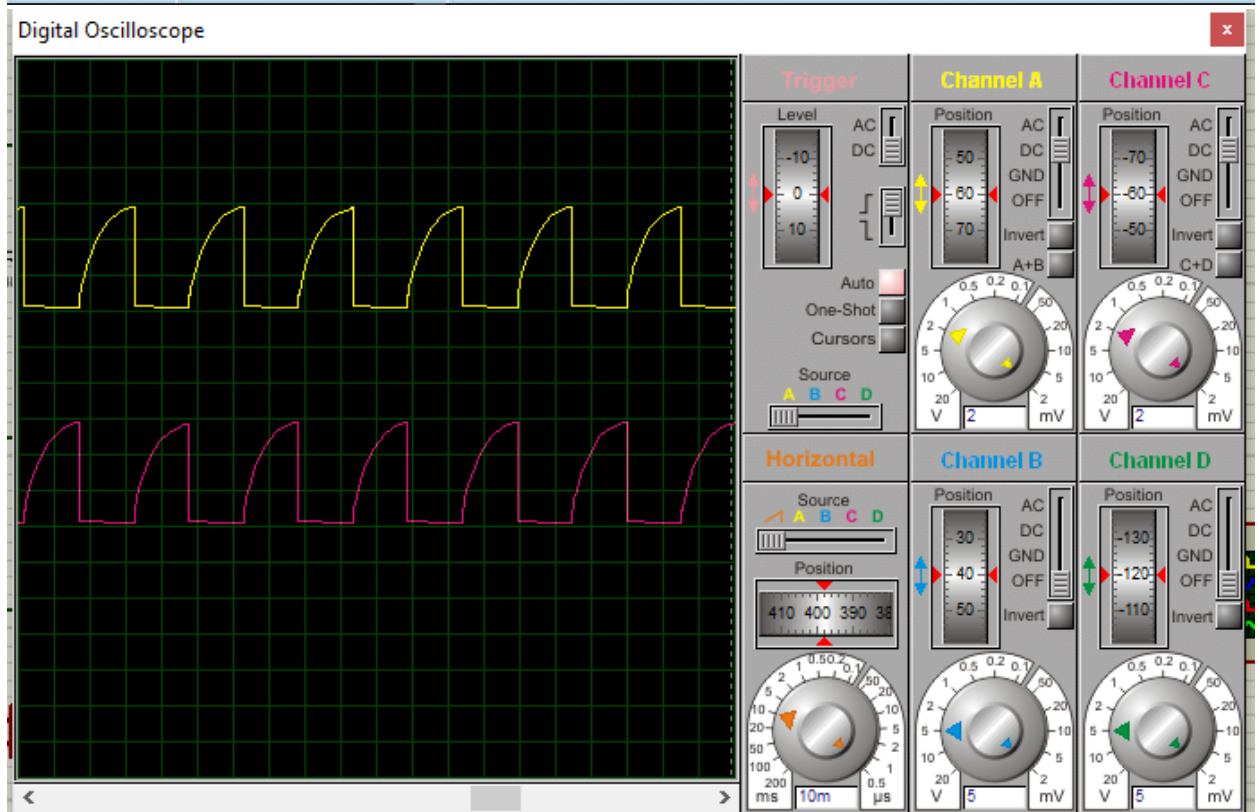


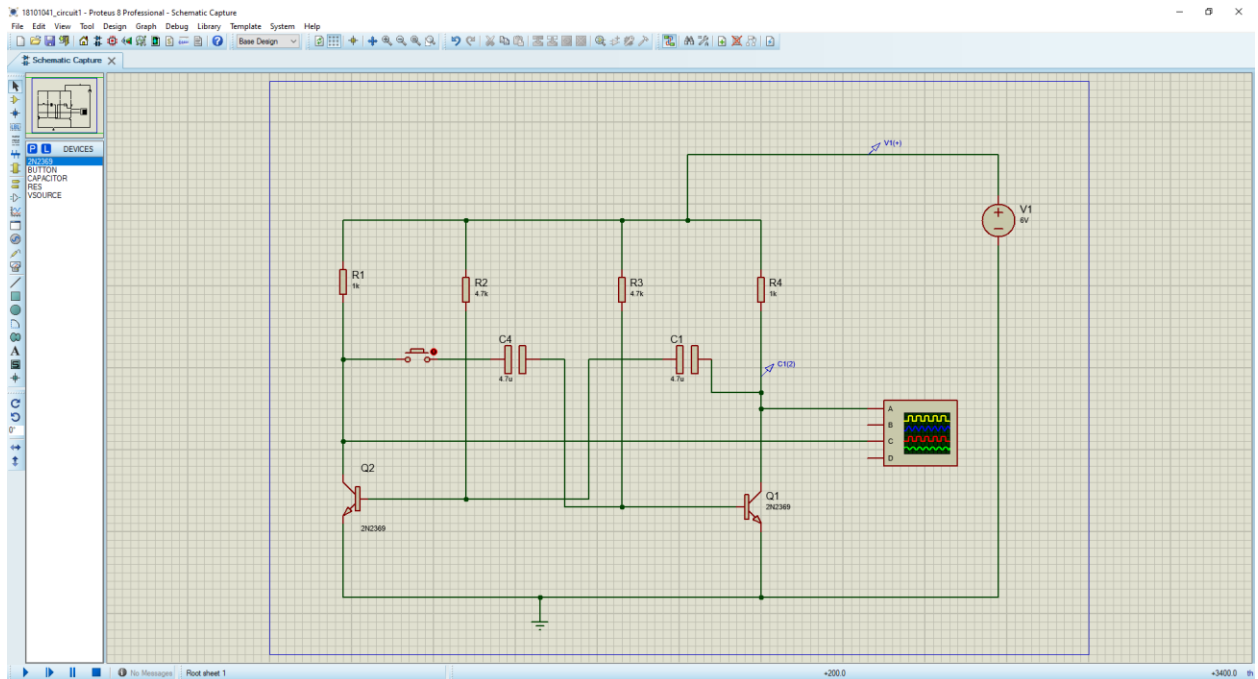



Brac University

Lab Assignment 06

Student Name	Sowat Hossain Rafi
Student ID Number	18101140
Section	01
Course Code	CSE350
Course Title	Digital Electronics and Pulse Techniques



18101041

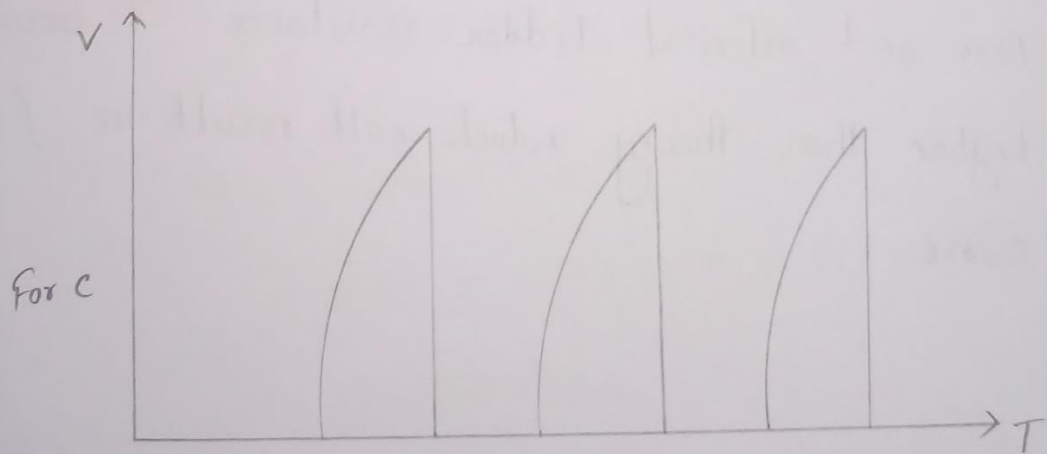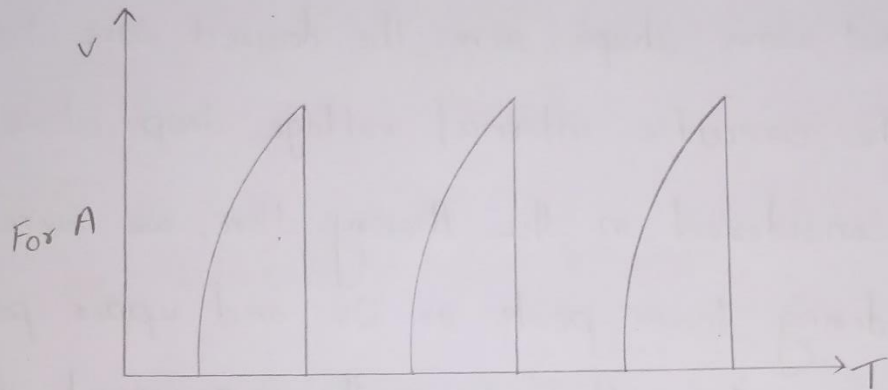Answer - 01

18101041

Answer-02

There are some deviation in the experimental output wave shape from the desired wave because of the circuit's internal voltage drop which was not considered in the theory. Here, we were considering lower peak as 0V and upper peak as V_{cc} or 6V . However, in the experiment, from the digital oscilloscope we got 0.25V as lower peak and 5.8V as upper peak. Moreover, due to system loss and internal hidden resistance τ becomes higher than theory which will result in flatter curve.

18101041

Date.....

Answer - 03

The time period of the experimental wave is similar to the calculated wave.

Here,

For theoretical or calculated wave

$$\begin{aligned}t_1 &= 0.69 \times C_1 \times R_3 \\&= 0.69 \times 4.7 \times 10^{-6} \times 4.7 \times 10^3 \\&= 0.0152421 \text{ s} \\&= 15.2421 \text{ ms.}\end{aligned}$$

$$\begin{aligned}t_2 &= 0.69 \times C_2 \times R_2 \\&= 0.69 \times 4.7 \times 10^{-6} \times 4.7 \times 10^3 \\&= 0.0152421 \text{ s} \\&= 15.2421 \text{ ms.}\end{aligned}$$

18101041

$$\begin{aligned}\text{Time period, } T &= t_1 + t_2 \\ &= (15.2421 + 15.2421) \text{ ms} \\ &= 30.4842 \text{ ms.}\end{aligned}$$

From Proteus, .

we got Time period, $T_p = 30.52 \text{ ms.}$

So, we can say that the time period of experimental wave and calculated wave is almost same.

Answer-04

It can be possible to use the above multivibrator to create variable frequency square wave if we use variable resistor or variable capacitor. We know that frequency of a square wave is dependent on the time period. In the multivibrator t_1 and t_2 both depends on the resistor and capacitor on the circuit. In this way, we can create frequency square wave.

18101041

Answer - 05

We can change the duty cycle of the circuit.
by changing the value of the resistances. or
capacitors.