

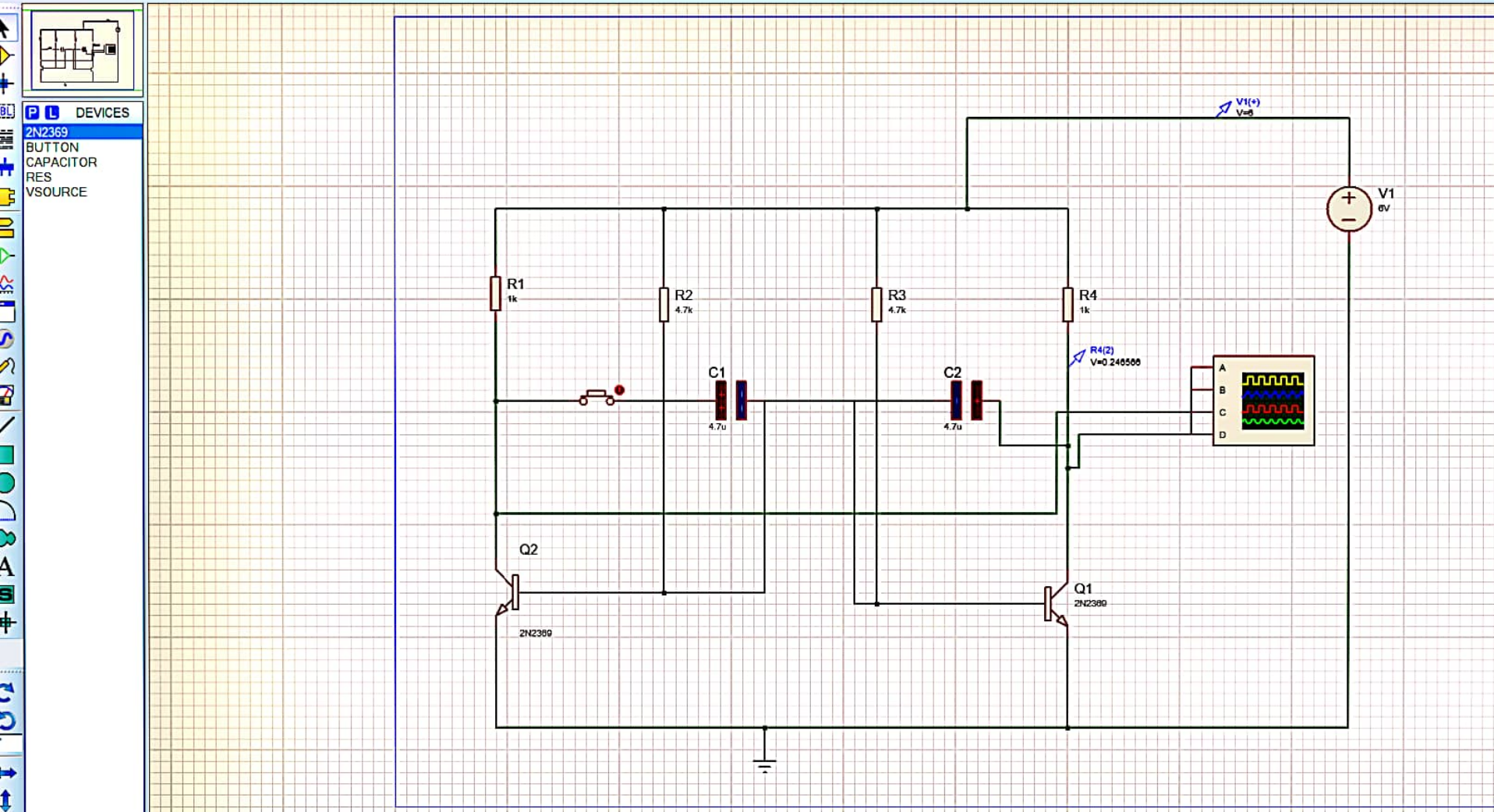


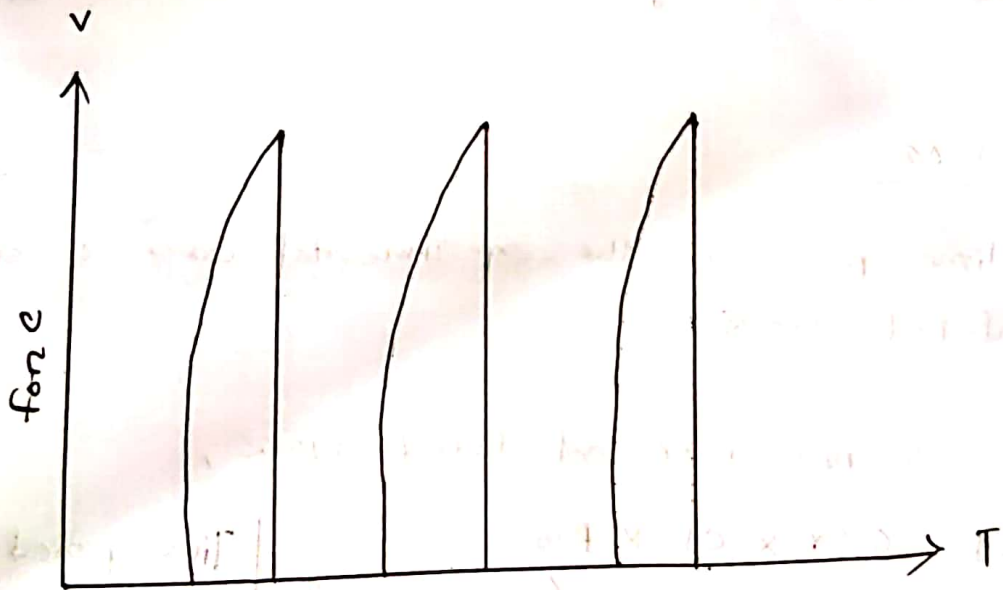

Schematic Capture X

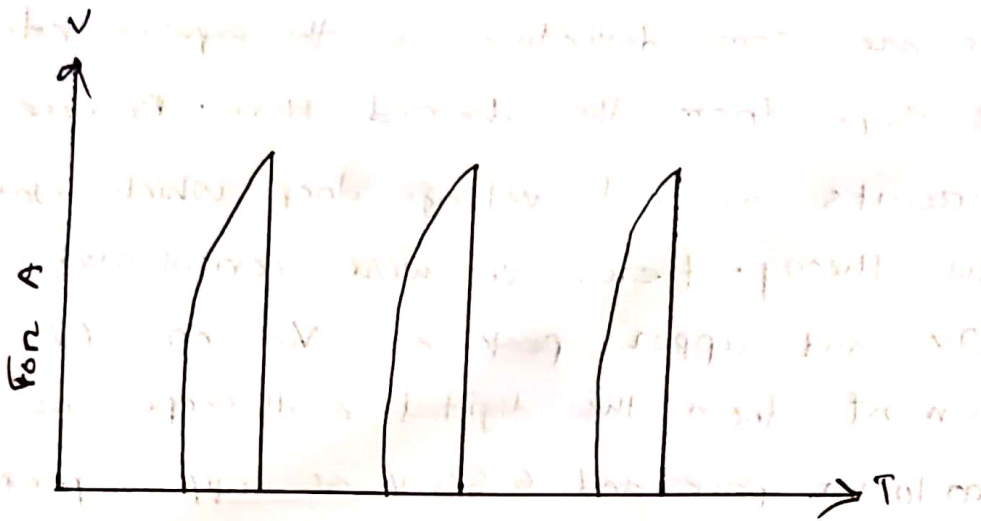

Answer 01



Answer 02:-

There are some deviation in the experimental output wave shape from the desired wave. Because of the the circuit's internal voltage drop which was not considered in the theory. Here, we were considering lower peak as 0V and upper peak as V_{CC} or 6V. But, in the experiment from the digital oscilloscope we got 0.25V as lower peak and 5.85V as upper peak. Due to system loss and internal hidden resistance C_T becomes higher than theory which will result in flatter curve.

Answer 03

The time period of the experimental wave is similar to the calculated wave.

For theoretical or calculated wave,

$$\begin{aligned}t_1 &= 0.69 \times C_1 \times R_3 \\&= 0.69 \times 4.7 \times 10^{-6} \times 4.7 \times 10^3 \\&= 15.242 \text{ ms}\end{aligned}$$

$$\begin{aligned}t_2 &= 0.69 \times C_2 \times R_L \\&= 0.69 \times 4.7 \times 10^{-6} \times 4.7 \times 10^3 \\&= 15.242 \text{ ms}\end{aligned}$$

Time period,

$$\begin{aligned}C_T &= t_1 + t_2 \\&= 30.484 \text{ ms}\end{aligned}$$

Sowad Hossain Rati
1810440 (03)

from Proteus,

We got Time period, $T_p = 30.52 \text{ ms}$


\therefore We can say that the time period of experimental wave and calculated wave is almost the same.

Answer 04

It can be possible to use the above multivibrator to create variable frequency square wave if we use variable resistor on a variable capacitor. The frequency of a square wave is dependent on the time period. In the multivibrator t_1 and t_2 both depends on the resistor and capacitor on the circuit. By this way, we can create frequency square wave.

Answer 05

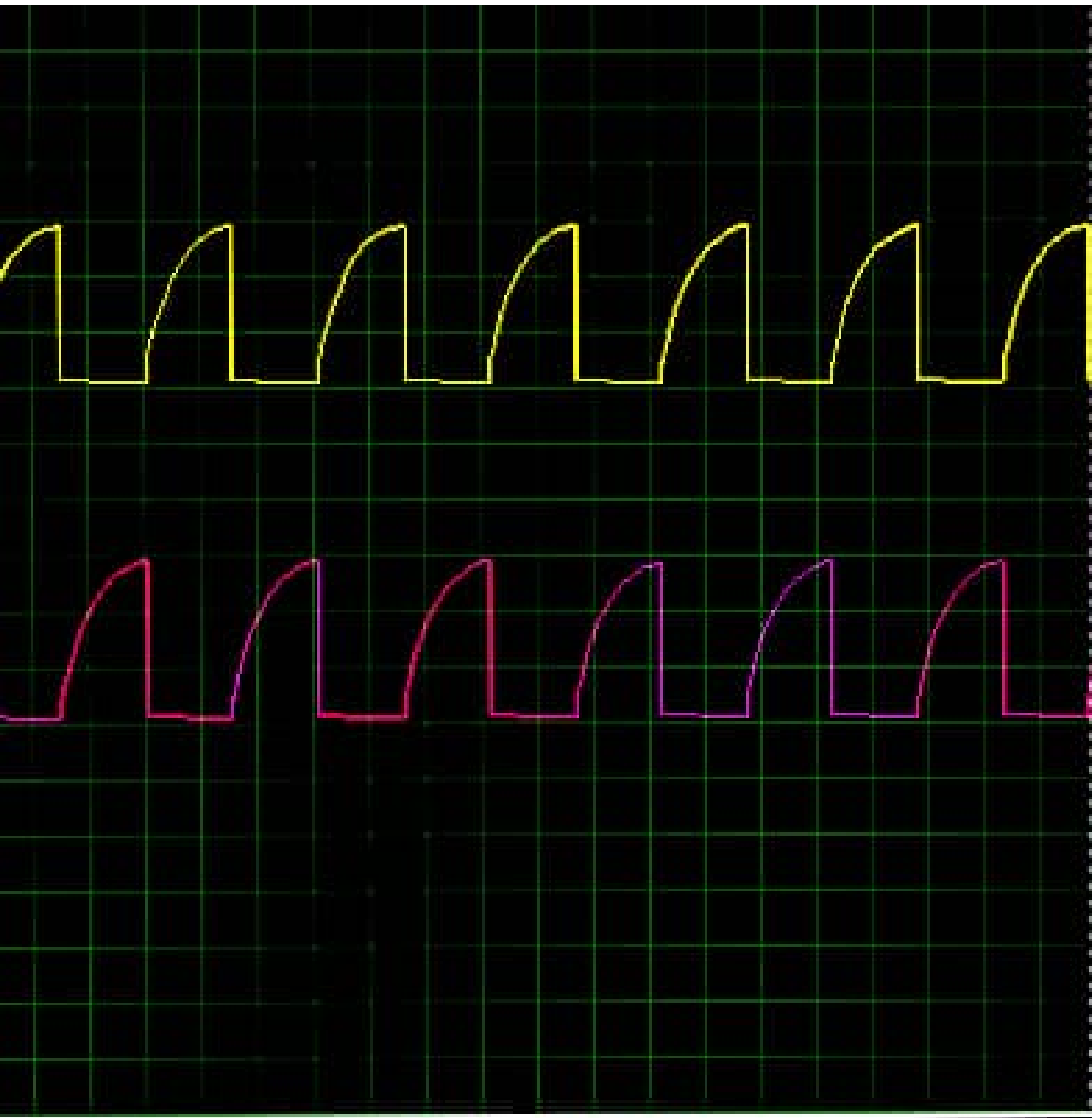We can change it by changing the value of the resistances or capacitors.



Trigger	Channel A	Channel C
<p>Level</p> <p>AC DC</p> <p>Auto One-Shot Cursors</p> <p>Source</p>	<p>Position</p> <p>AC DC GND OFF</p> <p>Invert A+B</p>	<p>Position</p> <p>AC DC GND OFF</p> <p>Invert C+D</p>
<p>Horizontal</p> <p>Source</p> <p>Position</p>	<p>Channel B</p> <p>Position</p> <p>AC DC GND OFF</p> <p>Invert</p>	<p>Channel D</p> <p>Position</p> <p>AC DC GND OFF</p> <p>Invert</p>